
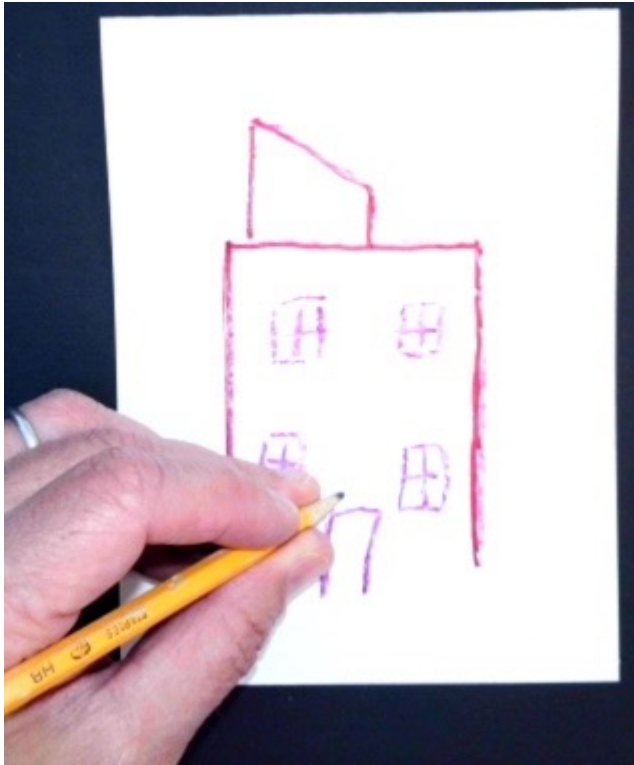


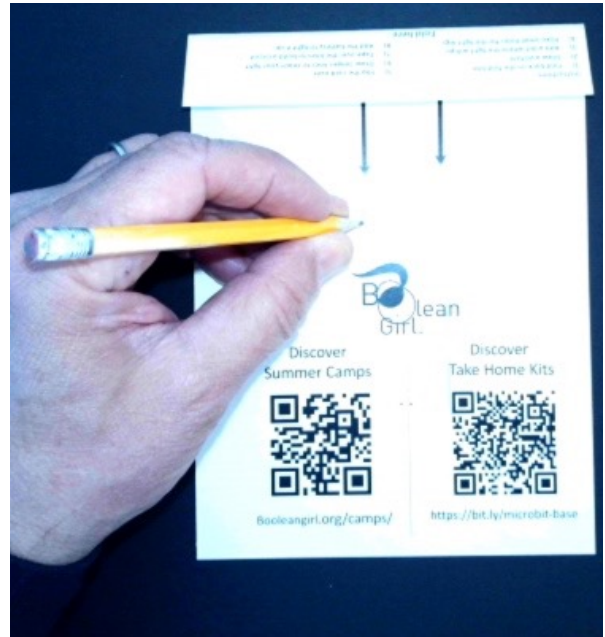
Draw a picture and add a dot where the light will go.




Poke two small holes for the light legs
Flip the card over and draw longer lines to reach your light



Tape over the lines to build a circuit

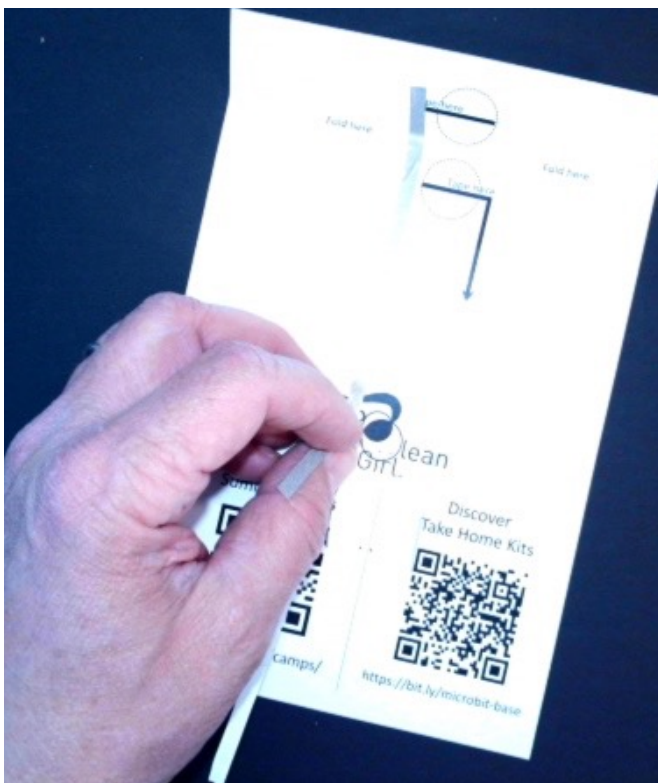

Add the battery to light it up.

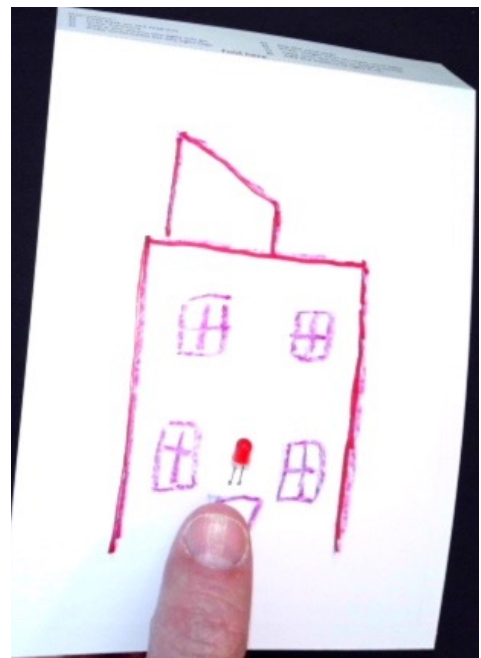

If it does not work, flip the battery over.